

# Additional material

## Chapter 2

### SECTION G Applications of equations to electrical circuits

By the end of this section you will be able to:

- ▶ state Kirchhoff's laws
- ▶ apply Kirchhoff's laws to electrical circuits
- ▶ solve simultaneous equations resulting from Kirchhoff's laws
- ▶ solve simultaneous equations using a computer algebra system

### G1 Modelling electrical circuits


If you are undertaking an electrical-related discipline then you may have covered Kirchhoff's laws in an electrical principles module. However, if you have not covered these laws then 2.7 and 2.8 give Kirchhoff's current and voltage laws respectively.

Kirchhoff's current law states

2.7 current entering a node = current leaving a node

For Fig. 43:

$$i_1 = i_2 + i_3 + i_4$$

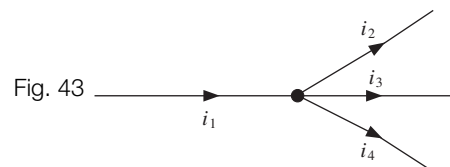


#### Example 20

Obtain equations relating the currents  $i_1$ ,  $i_2$ ,  $i_3$ ,  $i_4$  and  $i_5$  of Fig. 44.

Solution

All the currents apart from  $i_5$  are entering the node, therefore

$$i_5 = i_1 + i_2 + i_3 + i_4$$

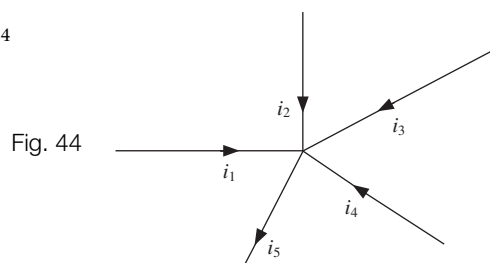

## 2

Kirchhoff's voltage law states

**2.8** applied voltage = sum of the voltage drops across each component in a loop

For the circuit of Fig. 45 we have

$$v = v_1 + v_2 + v_3$$

Ohm's law states that:

**2.9**  $v = iR$

where  $i$  is the current flowing through the resistor  $R$  and  $v$  is the voltage across the resistor  $R$  (Fig. 46).

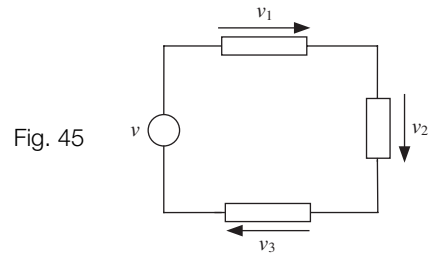


Fig. 45

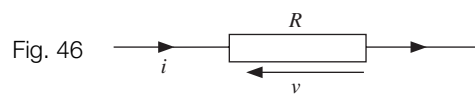


Fig. 46

### Example 21

Find the current  $i$  flowing through the circuit of Fig. 47.

**Solution**

Remember  $8 \text{ k}\Omega$  is  $8 \text{ kilo}\Omega$  and equals  $8 \times 10^3 \Omega$ . By applying Kirchhoff's voltage law **2.8** to the circuit of Fig. 47 we have

$$9 = (\text{voltage drop across } 8 \text{ k}\Omega) + (\text{voltage drop across } 10 \text{ k}\Omega)$$

$$= i(8\text{k}) + i(10\text{k}) \quad [\text{by applying Ohm's law}]$$

$$= i(18\text{k})$$

$$9 = (18 \times 10^3)i$$


Therefore

$$i = \frac{9}{18 \times 10^3} = 5 \times 10^{-4}$$

$$i = 0.5 \times 10^{-3} = 0.5 \text{ mA}$$

The unit mA is milliamps,  $10^{-3}$  A.

Fig. 47

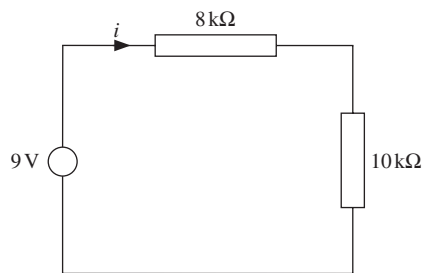


Consider the case where we have more than one loop in the circuit. A direction (normally clockwise) for the current is chosen. The current is positive when in this direction (clockwise) and negative when in the opposite direction (anticlockwise).

### Example 22

Determine the currents  $i_1$  and  $i_2$  in the circuit of Fig. 48.

Solution

Fig. 48

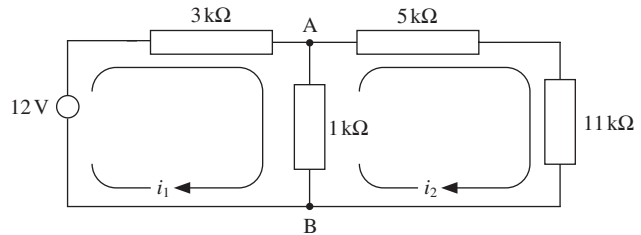

?

What current is flowing from A to B?

$$i_1 - i_2$$

because  $i_1$  and  $i_2$  are going in the opposite directions. Consider the two loops. By applying Kirchhoff's voltage law 2.8 to the first loop, we have

$$12 = (\text{voltage drop across } 3 \text{ k}\Omega) + (\text{voltage drop across } 1 \text{ k}\Omega)$$

$$\stackrel{\text{by 2.9}}{=} (3\text{k})i_1 + (1\text{k})(i_1 - i_2)$$

by 2.9

$$= (3\text{k})i_1 + (1\text{k})i_1 - (1\text{k})i_2$$

$$= (4\text{k})i_1 - (1\text{k})i_2$$

$$\dagger \quad 12 = (4 \times 10^3)i_1 - (1 \times 10^3)i_2$$

Applying 2.8 to the second loop:

$$\underbrace{0}_{\text{no voltage source in the second loop}} = (\text{voltage drop across } 5 \text{ k}\Omega) + (\text{voltage drop across } 11 \text{ k}\Omega) + (\text{voltage drop across } 1 \text{ k}\Omega)$$

$$0 = (5\text{k})i_2 + (11\text{k})i_2 + 1\text{k}(i_2 - i_1)$$

current from B to A

$$= (5\text{k} + 11\text{k} + 1\text{k})i_2 - (1\text{k})i_1$$

$$= (17\text{k})i_2 - (1\text{k})i_1$$

$$0 = (17 \times 10^3)i_2 - (1 \times 10^3)i_1$$

This gives

$$(1 \times 10^3)i_1 = (17 \times 10^3)i_2$$

$$\dagger\dagger \quad i_1 = 17i_2 \quad [\text{Cancelling } 10^3\text{'s}]$$

2.8 applied voltage = sum of voltage drops across each component in a loop

2.9  $v = iR$

### Example 22 *continued*

We need to solve the simultaneous equations obtained:

$$\dagger \quad 12 = (4 \times 10^3)i_1 - (1 \times 10^3)i_2$$

$$\dagger\dagger \quad i_1 = 17i_2$$

We can substitute  $i_1 = 17i_2$  into  $\dagger$ :

$$\begin{aligned} 12 &= (4 \times 10^3)17i_2 - (1 \times 10^3)i_2 \\ &= (67 \times 10^3)i_2 \end{aligned}$$

Hence

$$i_2 = \frac{12}{67 \times 10^3} = 1.79 \times 10^{-4} \text{ A}$$



**How can we find  $i_1$ ?**

Substitute  $i_2 = 1.79 \times 10^{-4}$  into  $i_1 = 17i_2$ :


$$\begin{aligned} i_1 &= 17 \times (1.79 \times 10^{-4}) \\ &= 3.04 \times 10^{-3} \text{ A} \end{aligned}$$

We have  $i_1 = 3.04 \text{ mA}$  and  $i_2 = 0.18 \text{ mA}$ .

If we consider more than two loops in a circuit then we can set up the equations using Kirchhoff's and Ohm's laws as above. However as for solving these equations, it is easier to use modern technology since it eradicates the drudgery out of the calculations. In the example below we have used a computer algebra system (MAPLE). It might be more convenient to use a graphical calculator because of its portability.
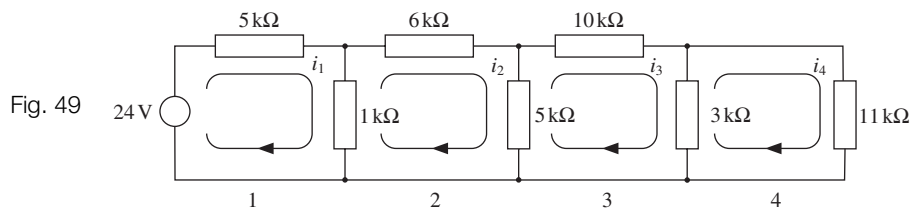
### Example 23

Obtain the values of the currents  $i_1$ ,  $i_2$ ,  $i_3$  and  $i_4$  in the circuit of Fig. 49.



**Solution**

Considering each loop separately.

Example 23 *continued*

Loop 1: Applying 2.8 we have

$$\begin{aligned} 24 &= (\text{voltage drop across } 5 \text{ k}\Omega) + (\text{voltage drop across } 1 \text{ k}\Omega) \\ &= (5\text{k})i_1 + (1\text{k})(i_1 - i_2) \quad [\text{by } 2.9] \\ &= (6\text{k})i_1 - (1\text{k})i_2 \\ 24 &= (6 \times 10^3)i_1 - (1 \times 10^3)i_2 \end{aligned}$$

Loop 2: Similarly

$$\begin{aligned} 0 &= (\text{voltage drop across } 6 \text{ k}\Omega) + (\text{voltage drop across } 5 \text{ k}\Omega) \\ &\quad + (\text{voltage drop across } 1 \text{ k}\Omega) \\ &= (6\text{k})i_2 + (5\text{k})(i_2 - i_3) + (1\text{k})(i_2 - i_1) \\ &= (12\text{k})i_2 - (1\text{k})i_1 - (5\text{k})i_3 \\ 0 &= -(1 \times 10^3)i_1 + (12 \times 10^3)i_2 - (5 \times 10^3)i_3 \end{aligned}$$

Loop 3: We have

$$\begin{aligned} 0 &= (\text{voltage drop across } 10 \text{ k}\Omega) + (\text{voltage drop across } 3 \text{ k}\Omega) \\ &\quad + (\text{voltage drop across } 5 \text{ k}\Omega) \\ &= (10\text{k})i_3 + (3\text{k})(i_3 - i_4) + (5\text{k})(i_3 - i_2) \\ &= (18\text{k})i_3 - (3\text{k})i_4 - (5\text{k})i_2 \\ 0 &= -(5 \times 10^3)i_2 + (18 \times 10^3)i_3 - (3 \times 10^3)i_4 \end{aligned}$$

Loop 4:

$$\begin{aligned} 0 &= (\text{voltage drop across } 11 \text{ k}\Omega) + (\text{voltage drop across } 3 \text{ k}\Omega) \\ &= (11\text{k})i_4 + (3\text{k})(i_4 - i_3) \\ &= (14\text{k})i_4 - (3\text{k})i_3 \\ 0 &= -(3 \times 10^3)i_3 + (14 \times 10^3)i_4 \end{aligned}$$

Combining these four equations gives

$$\begin{aligned} (6 \times 10^3)i_1 - (1 \times 10^3)i_2 &= 24 \\ -(1 \times 10^3)i_1 + (12 \times 10^3)i_2 - (5 \times 10^3)i_3 &= 0 \\ -(5 \times 10^3)i_2 + (18 \times 10^3)i_3 - (3 \times 10^3)i_4 &= 0 \\ -(3 \times 10^3)i_3 + (14 \times 10^3)i_4 &= 0 \end{aligned}$$

2.8 applied voltage = sum of voltage drops across each component in a loop

2.9  $v = iR$

### Example 23 *continued*

Solving these using MAPLE we obtain ( $10^3$  can also be replaced by e3 in MAPLE)

$$\begin{aligned} > \text{eqn1} := (6 \cdot 10^3) \cdot i[1] - (1 \cdot 10^3) \cdot i[2] = 24; \\ \text{eqn 1} := 6000 i_1 - 1000 i_2 = 24 \end{aligned}$$

$$\begin{aligned} > \text{eqn2} := - (1 \cdot 10^3) \cdot i[1] + (12 \cdot 10^3) \cdot i[2] - (5 \cdot 10^3) \cdot i[3] = 0; \\ \text{eqn 2} := - 1000 i_1 + 12000 i_2 - 5000 i_3 = 0 \end{aligned}$$

$$\begin{aligned} > \text{eqn3} := - (5 \cdot 10^3) \cdot i[2] + (18 \cdot 10^3) \cdot i[3] - (3 \cdot 10^3) \cdot i[4] = 0; \\ \text{eqn 3} := - 5000 i_2 + 18000 i_3 - 3000 i_4 = 0 \end{aligned}$$

$$\begin{aligned} > \text{eqn4} := - (3 \cdot 10^3) \cdot i[3] + (14 \cdot 10^3) \cdot i[4] = 0; \\ \text{eqn 4} := - 3000 i_3 + 14000 i_4 = 0 \end{aligned}$$

$$\begin{aligned} > \text{evalf} (\text{solve} (\{\text{eqn1}, \text{eqn2}, \text{eqn3}, \text{eqn4}\})); \\ \{i_1 = .004064145714, i_3 = .0001108691348, i_4 = .00002375767175, \\ i_2 = .0003848742823\} \end{aligned}$$

Rounding to 2 d.p. we have

$$i_1 = 4.06 \text{ mA}, i_2 = 0.38 \text{ mA}, i_3 = 0.11 \text{ mA} \text{ and } i_4 = 0.02 \text{ mA}$$

## SUMMARY

Kirchhoff's current law:

$$2.7 \quad \text{current entering a node} = \text{current leaving a node}$$

Kirchhoff's voltage law:

$$2.8 \quad \text{applied voltage} = \text{sum of voltage drops across each component in a loop}$$


Ohm's law:

$$2.9 \quad v = iR$$

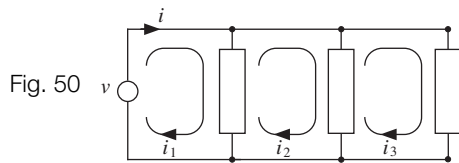
### Exercise 2(g)

Solutions are given at the end of this additional material. Complete solutions are in this website.


- 1** Ascertain an expression relating the currents  $i$ ,  $i_1$ ,  $i_2$  and  $i_3$  for the circuit of Fig. 50.



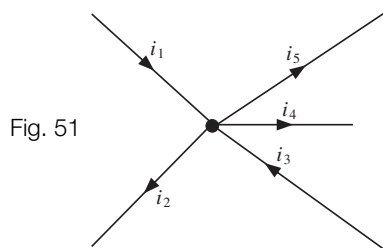
- 2** Write an expression relating the currents  $i_1$ ,  $i_2$ ,  $i_3$ ,  $i_4$  and  $i_5$  for the circuit of Fig. 51.



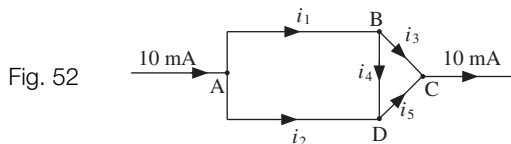
- 3** Obtain four relationships, one for each node A, B, C, D, between the currents  $i_1$ ,  $i_2$ ,  $i_3$ ,  $i_4$  and  $i_5$  for the circuit of Fig. 52.



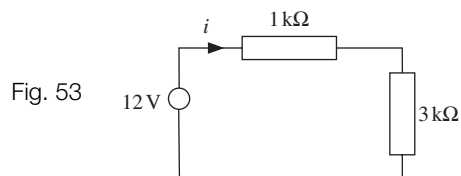
- 4** Find the current  $i$  flowing through the circuit of Fig. 53.



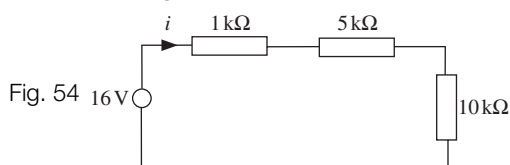
- 5** Obtain a value for the current  $i$  of the circuit of Fig. 54.



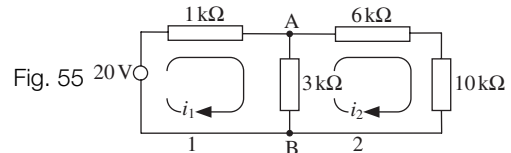
- 6** Obtain the values of the currents  $i_1$  and  $i_2$  for the circuit of Fig. 55.



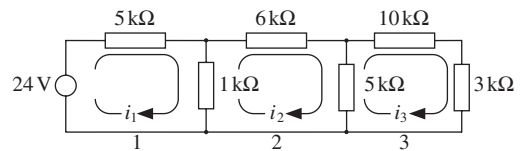
- 7** Find the currents  $i_1$ ,  $i_2$  and  $i_3$  shown in the circuit of Fig. 56.



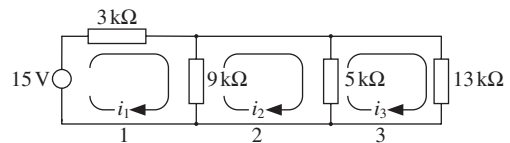- 8** Establish the values of the currents  $i_1$ ,  $i_2$  and  $i_3$  for the circuit of Fig. 57.



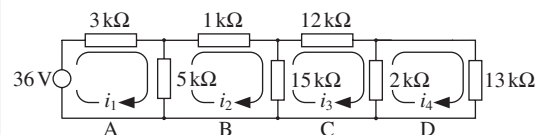- 9** Find the values of the currents  $i_1$ ,  $i_2$ ,  $i_3$  and  $i_4$  for the circuit of Fig. 58.



- 10** Determine the values of currents  $i_1$ ,  $i_2$  and  $i_3$  for the circuit of Fig. 59.

